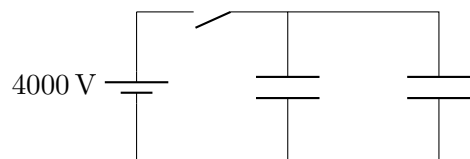


Physics 158 Circuits Problem Bank

Problem 1



Time Independent Circuits

Time Dependent Circuits

RLC Circuits

AC Circuits