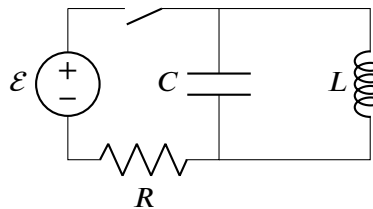


Physics 158 Written Homework 2

Problem 1

Difficulty: ★☆☆

The LRC circuit below is constructed with a 12 V battery, $6\ \Omega$ resistor, $5\ \mu\text{F}$ capacitor, and 0.5 mH inductor.



If the switch has been closed for a long time and is suddenly opened, find:

- How much current is flowing through the inductor just after the switch has been opened.
- How much charge is stored on the capacitor at the instant the switch is opened.
- The initial energy in the circuit.
- The maximum current in the circuit.
- How often the capacitor attains a max charge per second (only consider the absolute value of the charge).
- How much power is dissipated in the circuit after 40 seconds.

Problem 2

Difficulty: ★☆☆

A 2 F capacitor, 0.25 H inductor, and a $100\ \Omega$ resistor are connected in series with a voltage source $v(t) = 25 \cos(80t - \frac{\pi}{2})$

- What is the impedance of this circuit?
- What is the peak current?
- What is the peak voltage across each element?

Problem 3

Difficulty: ★☆☆

A coil with $L = 88 \text{ mH}$ and unknown resistance, and a capacitor ($C = 0.94 \mu\text{F}$) are connected in series with an alternating EMF operating at a frequency $= 930 \text{ Hz}$. If the phase constant between the applied voltage and the current is $+75^\circ$, what is the resistance R of the coil?

Problem 4

Difficulty: ★★☆☆

Mystery RLC circuit: You are given an RLC circuit with elements connected in series. Values of R , L and C are unknown. You have at your disposal a source of AC voltage with $V_{\text{RMS}} = 8 \text{ V}$ and a tunable frequency ω . You also have an Ammeter which measures the RMS current I_{RMS} and the power factor $\cos \phi$.

Suppose you measured I_{RMS} as a function of frequency and found that the maximum RMS current occurs at $\omega_0 = 12.5 \text{ kHz}$ and is equal to 40 mA .

- What is the resistance, R ? What does this tell you about L and C ?
- What is the power factor at $\omega = \omega_0$?
- In addition you find that at $\omega_1 = 17 \text{ kHz}$ the power factor is 0.5 . Based on this information, what are the values of L and C ?

Problem 5

Difficulty: ★★☆☆

An AC circuit is connected in series with a resistor, capacitor, and an inductor with values of 30Ω , $2 \mu\text{F}$, and 2 H . If the circuit has an impedance of $Z = 220 \Omega$ what are all of the possible frequency values, ω ?

Problem 6

Difficulty: ★★☆☆

Consider a plastic ring of radius $R = 50.0 \text{ cm}$ on which there are two charged beads as shown in the figure below. Bead 1 has $q_1 = +2.00 \mu\text{C}$ and is fixed in place on the x -axis. Bead 2 has $q_2 = +6.0 \mu\text{C}$ and can be moved along the ring.

- Determine the positive angle θ for q_2 which can produce a net Electric field of magnitude $E = 2.00 \times 10^5 \text{ N/C}$ at the centre of the ring?
- Is there any negative angle θ for q_2 which can produce a net Electric field of magnitude $E = 2.00 \times 10^5 \text{ N/C}$ at the centre of the ring? If so, calculate that angle.

